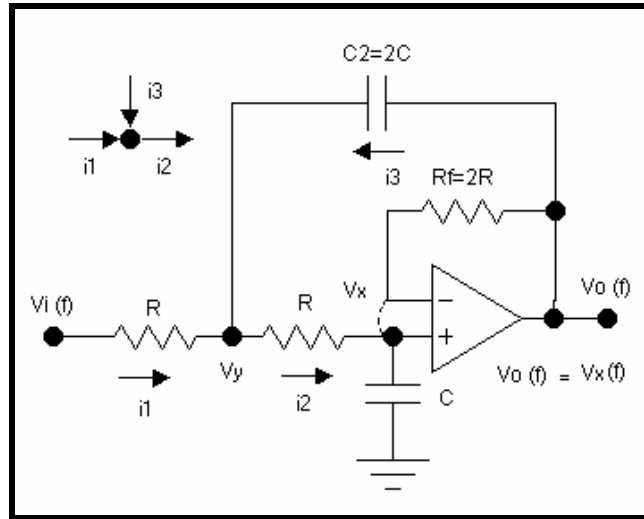


FILTRO PASABAJAS DE -40 db/dec



a. Hallar $A_v(w) = f(R, C, w)$

$$V_x(w) = \frac{Z_c}{R + Z_c} V_y(w) \quad \rightarrow \quad V_x(w) = \frac{1}{R + \frac{1}{jwC}} V_y(w) \quad \rightarrow$$

$$V_x(w) = \frac{1}{\frac{jwC}{jwRC + 1}} V_y(w)$$

$$V_x(w) = \frac{1}{jwRC + 1} V_y(w) \quad (1)$$

$$i_2 = i_1 + i_3$$

$$\frac{V_y}{R} - \frac{V_x}{R} = \frac{V_i}{R} - \frac{V_y}{R} + \frac{V_x}{\frac{1}{2jwC}} - \frac{V_y}{\frac{1}{2jwC}} \quad \rightarrow \quad \frac{V_y}{R} - \frac{V_x}{R} = \frac{V_i}{R} - \frac{V_y}{R} + 2jwCV_x - 2jwCV_y$$

$$\frac{V_y}{R} + \frac{V_y}{R} + 2jwCV_y = \frac{V_i}{R} + \frac{V_x}{R} + 2jwCV_x \quad \rightarrow \quad V_y \left(\frac{2}{R} + 2jwC \right) = \frac{V_i + V_x + 2jwCRV_x}{R}$$

$$V_y(w) = \frac{\frac{V_i + V_x + 2jwCRV_x}{R}}{\frac{2 + 2jwRC}{R}} \quad \rightarrow \quad V_y(w) = \frac{V_i + V_x(1 + 2jwCR)}{2 + 2jwRC} \quad \rightarrow \quad V_x(w) = V_o(w)$$



$$V_y(w) = \frac{V_i(w) + V_o(w)(1 + 2jwCR)}{2 + 2jwRC} \quad (2)$$

Reemplazo 2 en 1

$$V_x(w) = \frac{1}{jwRC + 1} \left[\frac{V_i(w) + V_o(w)(1 + 2jwCR)}{2 + 2jwRC} \right] \rightarrow V_x(w) = V_o(w)$$

$$V_o(w) = \frac{1}{jwRC + 1} \left[\frac{V_i + V_o(1 + 2jwCR)}{2 + 2jwRC} \right]$$

$$(jwRC + 1)(2 + 2jwRC)V_o(w) = V_i + V_o(1 + 2jwCR)$$

$$(jwRC + 1)(2 + 2jwRC)V_o(w) - V_o(1 + 2jwCR) = V_i(w)$$

$$V_o(w)[(jwRC + 1)(2 + 2jwRC) - (1 + 2jwCR)] = V_i(w)$$

$$V_o(w) = \frac{1}{2(jwRC + 1)^2 - (1 + 2jwCR)} V_i(w) \rightarrow$$

$$\frac{V_o(w)}{V_i(w)} = \frac{1}{2(jwRC + 1)^2 - (1 + 2jwCR)}$$

$$A_v(w) = \frac{1}{2(jwRC + 1)^2 - (1 + 2jwCR)} \rightarrow A_v(w) = \frac{1}{-2w^2R^2C^2 + 4jwRC + 2 - 1 - 2jwCR}$$

$$A_v(w) = \frac{1}{-2w^2R^2C^2 + 2jwRC + 1}$$

$$|A_v(w)| = \frac{1}{\sqrt{(1 - 2w^2R^2C^2)^2 + (2wRC)^2}}$$

$$\lim_{w \rightarrow \infty} |A_v(w)| = \frac{1}{\sqrt{(1 - \infty)^2 + (\infty)^2}} = \frac{1}{\infty} = 0 \quad (\text{Las frecuencias altas no pasan})$$

$$\lim_{w \rightarrow 0} |A_v(w)| = \frac{1}{\sqrt{(1 - 0)^2 + (0)^2}} = \frac{1}{1} = 1 \quad (\text{Las frecuencias bajas pasan})$$



b. Hallar w_c y f_c

$$\frac{1}{\sqrt{2}} = \frac{1}{\sqrt{(1-2w_c^2R^2C^2)^2 + (2w_cRC)^2}} \rightarrow \left(\sqrt{(1-2w_c^2R^2C^2)^2 + (2w_cRC)^2} = \sqrt{2} \right)^2$$

$$(1-2w_c^2R^2C^2)^2 + (2w_cRC)^2 = 2 \rightarrow$$

$$1 - 4w_c^2R^2C^2 + 4w_c^4R^4C^4 + 4w_c^2R^2C^2 = 2$$

$$1 + 4w_c^4R^4C^4 = 2 \rightarrow w_c^4 = \frac{1}{4R^4C^4} \rightarrow \sqrt[4]{w_c^4} = \sqrt[4]{\frac{1}{4R^4C^4}}$$

$$w_c = \frac{1}{\sqrt[4]{4RC}} \rightarrow \sqrt[4]{4} = \sqrt{2} \rightarrow \boxed{w_c = \frac{1}{\sqrt{2RC}}}$$

$$2\pi f_c = \frac{1}{\sqrt{2RC}} \rightarrow \boxed{f_c = \frac{1}{2\sqrt{2\pi RC}}}$$

c. Hallar $|A_v(f)| = f(f, f_c)$

$$|A_v(w)| = \frac{1}{\sqrt{(1-2w^2R^2C^2)^2 + (2wRC)^2}}$$

$$|A_v(w)| = \frac{1}{\sqrt{\left(1-2w^2\left(\frac{1}{w_c\sqrt{2}}\right)^2\right)^2 + \left(2w\left(\frac{1}{w_c\sqrt{2}}\right)\right)^2}} \rightarrow |A_v(w)| = \frac{1}{\sqrt{\left(1-\frac{2w^2}{2w_c^2}\right)^2 + \left(\frac{2w}{\sqrt{2}w_c}\right)^2}}$$

$$|A_v(w)| = \frac{1}{\sqrt{\left(1-\frac{w^2}{w_c^2}\right)^2 + \frac{4w^2}{2w_c^2}}} \rightarrow |A_v(w)| = \frac{1}{\sqrt{\left(1-\frac{w^2}{w_c^2}\right)^2 + \frac{2w^2}{w_c^2}}}$$

$$|A_v(f)| = \frac{1}{\sqrt{\left(1-\frac{(2\pi f)^2}{(2\pi f_c)^2}\right)^2 + \frac{2(2\pi f)^2}{(2\pi f_c)^2}}} \rightarrow \boxed{|A_v(f)| = \frac{1}{\sqrt{\left(1-\left(\frac{f}{f_c}\right)^2\right)^2 + 2\left(\frac{f}{f_c}\right)^2}}}$$



d. Dibujar $|A_v(f)|$ Vs f

$$|A_v(f)| = \frac{1}{\sqrt{\left(1 - \left(\frac{f}{f_c}\right)^2\right)^2 + 2\left(\frac{f}{f_c}\right)^2}}$$

$$A_v = 20 \log \left(\frac{V_o}{V_i} \right)$$

f	$ A_v(f) $	$ A_v(f) $ db
0	1	0
0.1 fc	0.999	0
0.5 fc	0.970	0
0.8 fc	0.842	-1
fc	0.707	-3
2 fc	0.242	-12
4 fc	0.062	-24
6 fc	0.027	-31
8 fc	0.015	-36
10 fc	0.009	-40